

# Adiabatic Logic

*Yasmine Badr*

NanoCAD Lab

A major part of the contents is from Reference 1

# Terminology

- **Reversible logic:**
  - circuits that have **one-to-one** mapping between vectors of inputs and outputs
- **“Adiabatic”** : from thermodynamics
  - Process in which there is no exchange of heat with the environment

# History


- Landauer (1961):
  - Logically irreversible operations in a physical computer necessarily dissipate energy
  - Logically reversible operations “can” be performed without dissipation
- Later, found that that a gate can work **energetically reversible** without the need to be **logically reversible**.

# Adiabatic Circuits

- Energy reused rather than just dissipated
- Power advantage

 
# Conventional CMOS

- **Constant voltage**
- Energy dissipated per transition  
 $= CV_{dd}^2/2$ 
  - Pull up: energy dissipated on PMOS
  - Pull down: charge dissipated via NMOS to ground
- Energy used only once



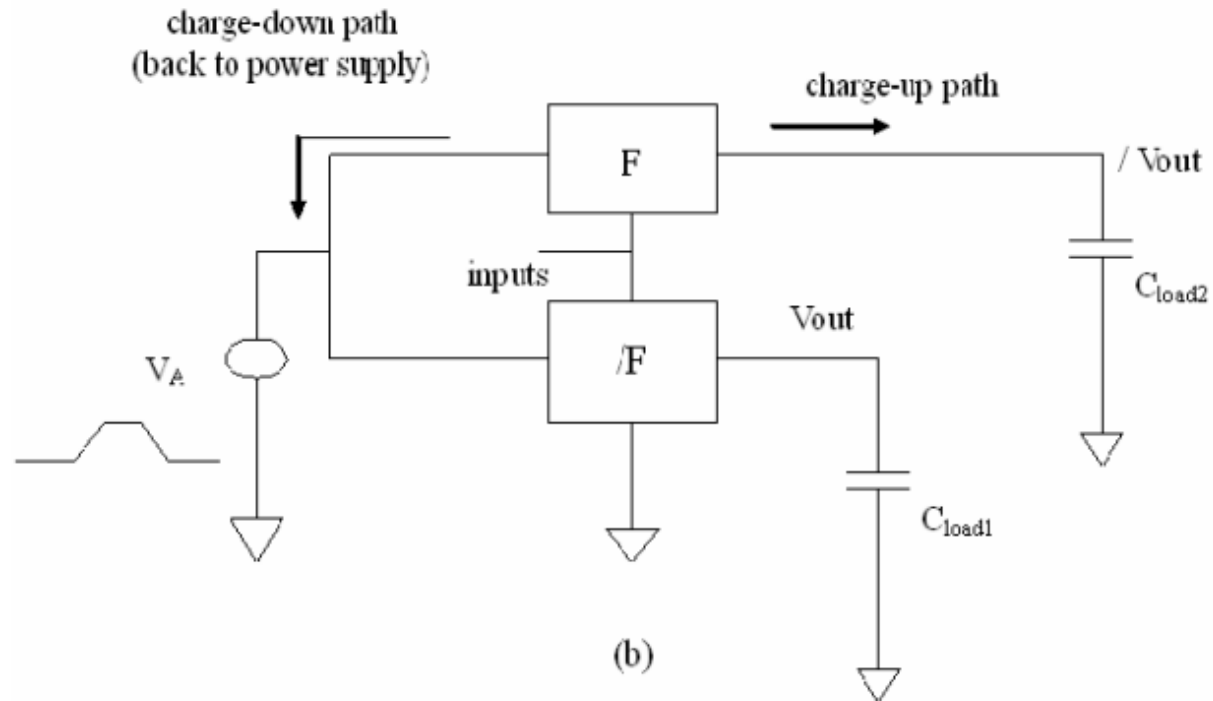
# Adiabatic Logic

- Supply is a **power clock** (ramp)
- Pull down path: to **power supply**


 
# Adiabatic Logic Energy Dissipation

- $i(t) = c \, dV/dt$   
 $= c \, V_{DD}/T$   
**(Constant Current)**
- Energy during transition time  $T$   
 $= I^2 * R * T$   
 $= R * C^2 * V_{DD}^2 / T$



# CMOS

- Dissipated energy in pull up and pull down  
=  $CV_{dd}^2$
- Depends on C and Vdd only

# Adiabatic

- Dissipated energy in charge and recovery  
=  $2 * R * C^2 * V_{dd}^2 / T$
- Depends on **size** of transistor and **T** as well
- Slower circuit is charged → less energy dissipation

$T > 2RC$  → Adiabatic has less energy dissipation if we assume activity factor of 1




# Adiabatic Logic Families



- Adiabatic system has:
  - *Digital core*: adiabatic gates
  - *Generator of power clock* signals
    - 4-phase power clock for cascaded gates
    - Efficient generation essential for high energy saving factor
- Two of the most popular
  - Efficient Charge Recovery Logic (ECRL)
  - Positive Feedback Adiabatic Logic (PFAL)
 
# 1-ECRL Inverter

- Logic implemented using NMOS
- 2 cross coupled PMOS to store info
- For a different function e.g. NAND
  - a series connection of 2 NMOS instead of  $N_F$ , using A and B as inputs.
  - 2 parallel transistors, having A' and B' as inputs instead of  $N_F$




# 1-ECRL Buffer/Inverter (cont'd)

  

- Input signal is shifted by 90 degrees w.r.t to the power clock

 
# 1-ECRL Buffer/Inverter (cont'd)

- Power clock ramping **up** from 0 to Vdd
- Out follows Power clock



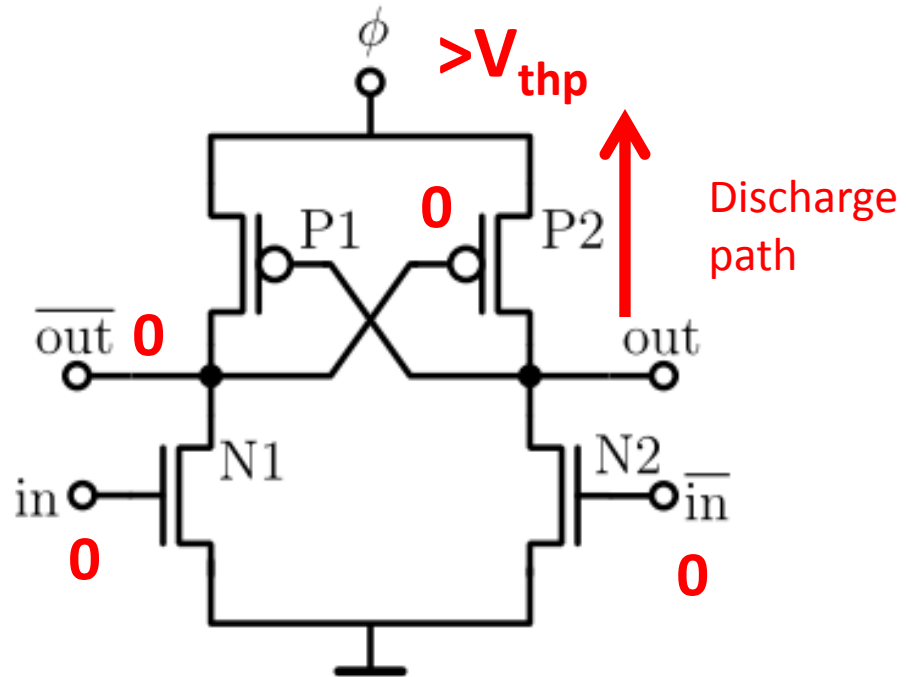
# 1- ECRL Buffer/Inverter (cont'd)

- Power clock ramping **down** from  $V_{dd}$  to zero
- Both inputs are now zero
  - Because preceding stage is now recovering energy
  - Not strictly complementary
- N1 and N2 off



 
# 1- ECRL Buffer/Inverter (cont'd)

- $\Phi < V_{th,p}$
- Fraction of energy  
=  $\frac{1}{2} C_{out} V_{th,p}^2$   
dissipated or reused  
next cycle according to  
succeeding input signal  
→ Quasi-adiabatic


 
# 2-PFAL Inverter/buffer

- Consists of:
  - Latch made of 2 cross-coupled inverters
  - Logic function




# ERCL vs PFAL

- ERCL: less number of transistors
- PFAL:
  - Functional block parallel to PMOS
  - less equivalent resistance
  - less energy dissipated ( $R * C^2 * V_{dd}^2 / T$ )


 
# 4-Phase Power clock for Cascade

- **More than 1 power clock** used to operate **adiabatic system**
  - ERCL and PFAL use 4-phase power clock  $\phi_0$ - $\phi_3$
- Because input has to be stable in evaluation phase
  - ERCL and PFAL:  $90^\circ$  phase shift between subsequent phases is obtained



# 4-Phase Power clock for Cascade (cont'd)

- 4 – Phases:
  - *Evaluate (E)*: outputs are evaluated from stable input signals
  - *Hold (H)*: outputs are kept stable to supply subsequent gate with stable input signal.
  - *Recover (R)*: Energy is recovered
  - *Wait (W)*: for symmetry reasons because symmetric signals are easier to generate

# Power Supply

- LC circuit
- Stepwise charging
  - Charging of output to VDD is not done abruptly, but is divided into N steps

# Cons and Pros

- Slower than conventional CMOS
- Requires special power supply
- Area (but we get function and its complement)
- + Less **Power** if high switching activity  
or disconnect system from power supply while  
idle (sleep transistors)

# References

1. **Teichmann**, Philip; Adiabatic Logic; Springer; 2012
2. Vitányi, P.; Time, space, and energy in reversible computing; *Proceedings of the 2nd conference on Computing frontiers, ACM, 2005*, 435-444
3. Pahlavan,B; Evaluation of Trends in Adiabatic Logic for Low Power Design  
[http://cutler.eecs.berkeley.edu/classes/icdesign/ee241\\_s06/projects/midterm/pahlavanghanadanskucha.pdf](http://cutler.eecs.berkeley.edu/classes/icdesign/ee241_s06/projects/midterm/pahlavanghanadanskucha.pdf)
4. Frank, M; Reversible Computing and Truly Adiabatic Circuits: Truly Adiabatic Circuits: The Next Great Challenge for Digital Engineering; 2006
5. Sanjay Kumar; Design Of Low Power Cmos Cell Structures Based On Adiabatic Switching Principle; Master Thesis; 2009