

Calibration of Setup and Hold Time for Latches and Flip-flops(II)


Chia-Hao Chang
Prof. Puneet Gupta

Outline

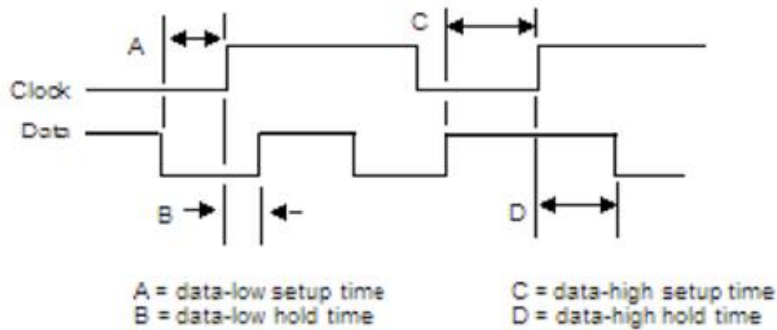
1. Definition of setup and hold time
2. Purpose for the constraints
3. Latches transient response example
4. Flip-Flops transient response example
5. References

Definition of Setup and Hold Time(1/2)

Setup and Hold Times Specification for Rising-Edge-Triggered Flip-Flop



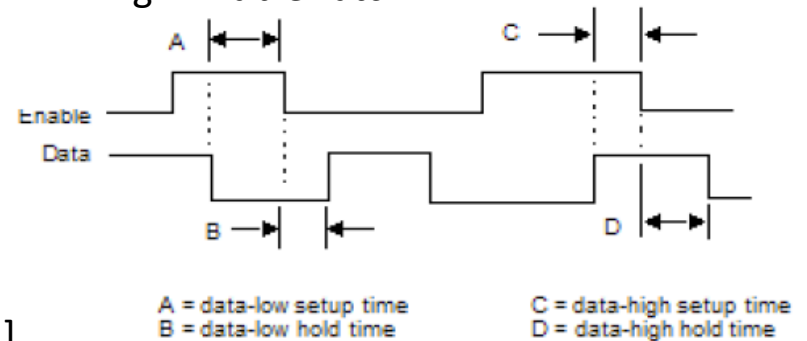
Setup and Hold Specification for High-Enable Latch



[1]

As the data setup time decrease and move toward the boundary of failure region, the clk-Q delay will increase.

 When it reach beyond the boundary, it will not be able to flip the Q signal to follow the D signal.





[2]

Setup and hold constraints(1/2)

The industrial methodology to calibrate setup and hold time is done by calibrating the nominal Clk-Q delay and search for the setup/hold time that gives the 1.1xnominal delay. The binary search is usually applied.

[3]

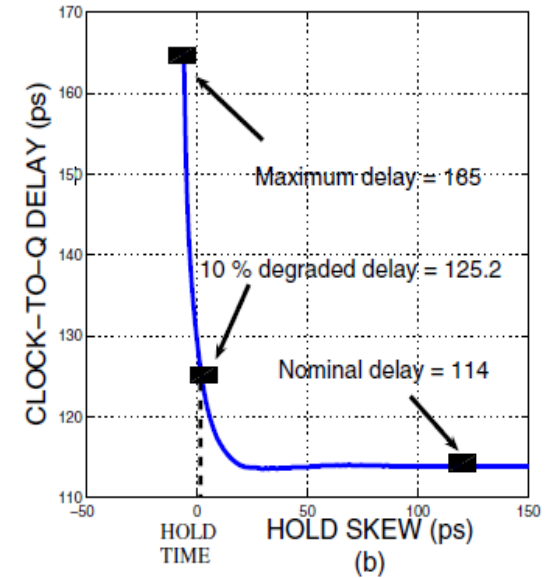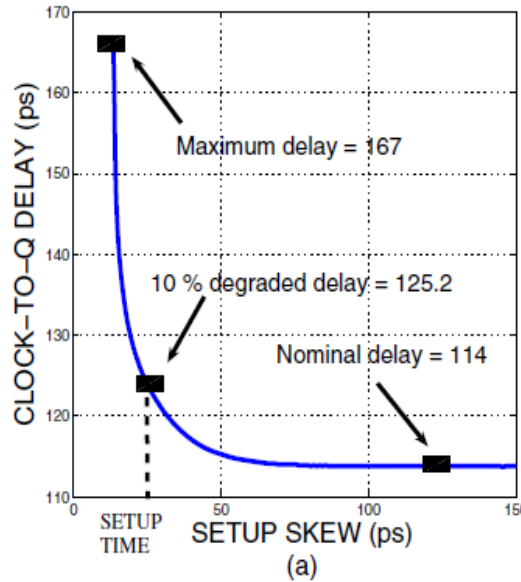



- In most lib file, calibrated for different sets of
 - Slope of CLK signal
 - Slope of Data signal

```
index_1("0.4, 0.57, 0.84"); /* Data transition Time*/
index_2("0.4, 0.57, 0.84"); /* Clock transition Time*/
values( /* 0.4 0.57 0.84 */ \
/* 0.4 */ "0.063, 0.093, 0.112", \
/* 0.57 */ "0.526, 0.644, 0.824", \
/* 0.84 */ "0.720, 0.839, 0.930");
```

...


[4]

Purpose of the constraints(1/2)

  


[5]

Setup time example

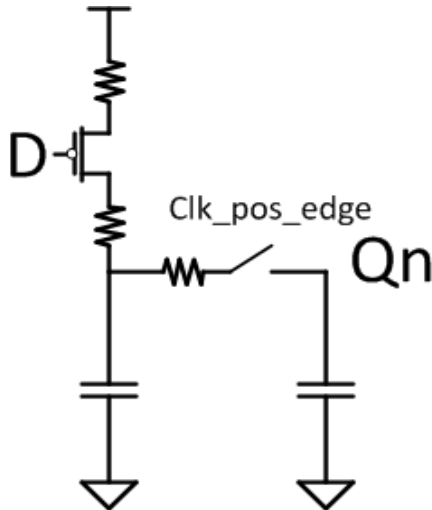


Hold time example

 

A delay of a gate is a function of the input slop




If there is a slope in controlling signal, then for some CMOS circuits both NMOS and PMOS might be turn on and increase the required time of charging and discharging

Latches transient response


 


The internal nodes are not yet full discharge before the enable signal goes $< v_t$

   
The internal node fail to compete with Q and the result is flipped back




D Flip-Flop transient response

 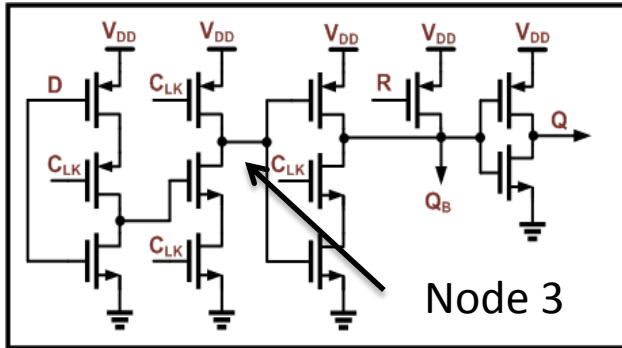

 Hold time Violation:
the Node 3 was raised
due to the arriving new
data



 Clock slope effect:
Same hold time, but steeper
Clk will yield a small Clk-Q
delay



Reference

- [1] W. Roethig, "Library Characterization and Modeling for 130 nm and 90 nm SOC Design," *Proceedings of the IEEE International SOC Conference*, pp. 383–386, September 2003.
- [2] S. Sundareswaran, "Statistical Characterization For Timing Sign-Off: From Silicon to Design and Back to Silicon," Doctorial thesis of the University of Texas at Austin, 2009
- [3] Salman, E.; Dasdan, A.; Taraporevala, F.; Kucukcakar, K.; Friedman, E.G.; , "Pessimism reduction in static timing analysis using interdependent setup and hold times," *Quality Electronic Design, 2006. ISQED '06. 7th International Symposium on* , vol., no., pp.6 pp.-164, 27-29 March 2006
- [4] J. Bhasker and Rakesh Chadha, "Static Timing Analysis for Nanometer Designs: A Practical Approach. Springer," first edition, April 2009.
- [5] K. Yang, "Clocking Methodology and Flip-Flops," EE215B lecture note, Winter 2010
- [6] Srivastava, S.; Roychowdhury, J.; , "Rapid and Accurate Latch Characterization via Direct Newton Solution of Setup/Hold Times," *Design, Automation & Test in Europe Conference & Exhibition, 2007. DATE '07* , vol., no., pp.1-6, 16-20 April 2007
- [7] Jan M. Rabaey, Anantha Chandrakasan, and Borivoje Nikolic', "Digital Integrated Circuit", Secnod Edition, 2002
- [8] Wikipedia, "Flip-flop (electronics)"
[http://en.wikipedia.org/wiki/Flip-flop_\(electronics\)](http://en.wikipedia.org/wiki/Flip-flop_(electronics))